

# Practicle 8

## Representing a given circuit diagram (expressed using Gates) in the form of Boolean expression

**To give Boolean expression of the given circuit diagram, we define each gate  $G_i$  separately, and finally ask for the value of the output  $G_1$**

```
In[23]:= G4 = ! a;  
G5 = ! c;  
G2 = a ∧ b;  
G3 = G4 ∧ G5 ∧ b;  
G1 = G2 ∨ G3;  
G1
```

```
Out[28]=  
(a && b) || (! a && ! c && b)
```

2.

```
In[29]:= G2 = A ∧ B ∧ C;  
G4 = ! C;  
G3 = A ∧ B ∧ G4;  
G5 = ! A;  
G6 = ! C;  
G7 = G5 ∧ B ∧ G6;  
G1 = G2 ∨ G3 ∨ G7;  
G1
```

```
Out[36]=  
(A && B && C) || (A && B && ! C) || (! A && B && ! C)
```